
LAB8 Homework

學號: E24116152 姓名:劉冠好

檔案名稱為 Lab8_學號.pdf, 若檔名格式錯誤或非.pdf 檔會扣

分!!

1-1. 設計一個 inverter, 電晶體長寬比如下

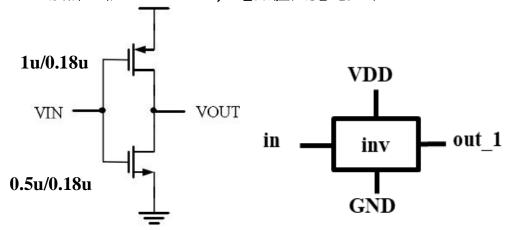


1-2. 請截取 terminal 顯示 job concluded 的圖

```
140.116.156.6 - PuTTY
                                                                          ×
 ***** Runtime Statistics (seconds)
                    time
                             # points
 op point
                                                          189 rev=
 transient
 readin
 errchk
 setup
                    0.00
 output
          peak memory used
                                   263.96 megabytes
          total cpu time
                                   0.05 seconds
                            30.41 seconds
13:36:18 05/13/2024
          total elapsed time
          job started at
          job ended at
                             13:36:49 05/13/2024
              ***** hspice job concluded
>info:
lic: Release hspice token(s)
lic: total license checkout elapse time:
lsicad6:/home/user2/vlsi24/vlsi2424/Lab8 E24116152 % wv &
```


三個元件都寫在 circiut.spi 一個檔案。

1-3. 請截取 WaveView 中 in 及 out_l 的波形

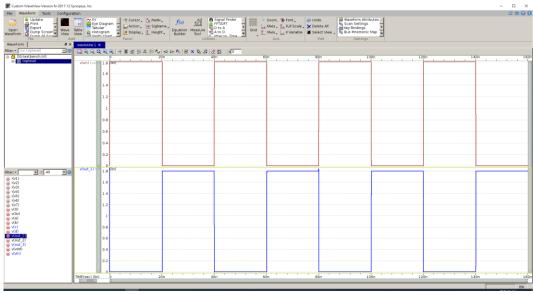


褐色為 in,藍色為 out_1。

2-1. 設計一個 NAND, 電晶體長寬比如下

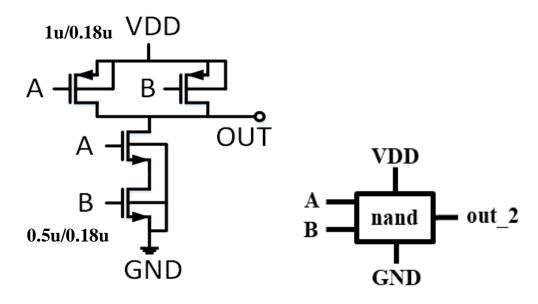


2-2. 請截取 terminal 顯示 job concluded 的圖

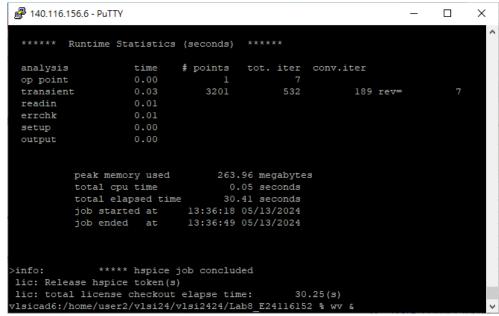


三個元件都寫在 circiut.spi 一個檔案。

2-3. 請截取 WaveView 中 A、B 及 out_2 的波形

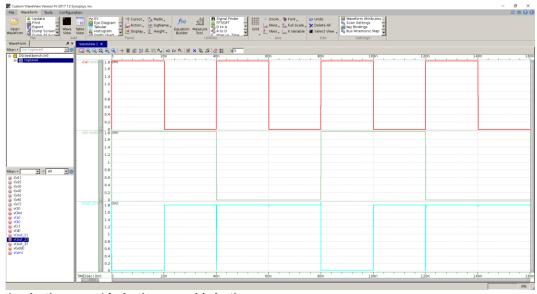


紅色為A,綠色為B,藍色為out_2。

3-1. 設計一個 NOR, 電晶體長寬比如下

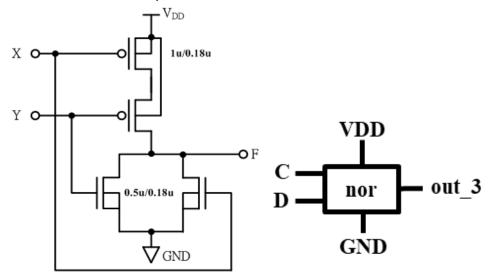


3-2. 請截取 terminal 顯示 job concluded 的圖

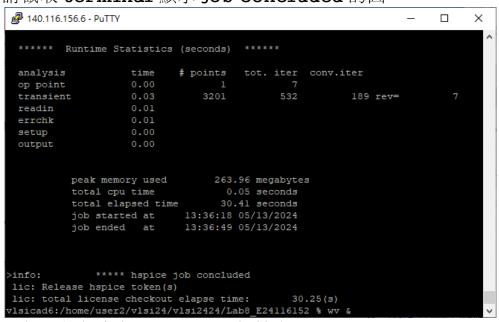

三個元件都寫在 circiut.spi 一個檔案。

3-3. 請截取 WaveView 中 C、D 及 out_3 的波形

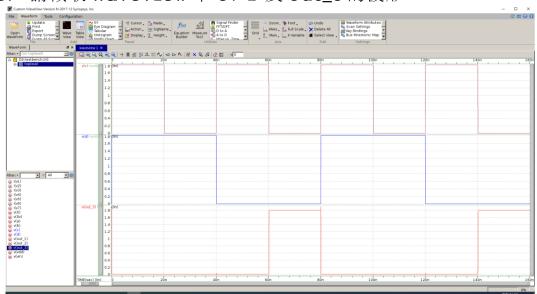

褐色為 C,藍色為 D,紅色為 out_3。

4. 結論/建議 (可寫可不寫,不影響作業評分,僅做為下次上課方式的參考) 講解得很清楚,沒什麼問題。